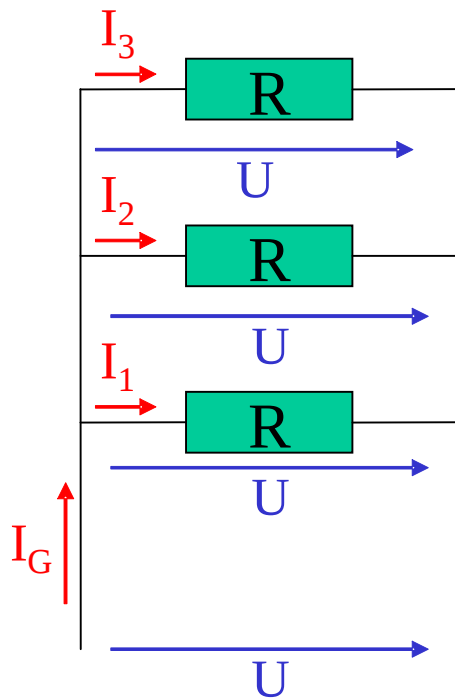



Parallel



$$I_G = I_1 + I_2 + I_3$$

$$U = U = U = U$$

Reihenschaltung

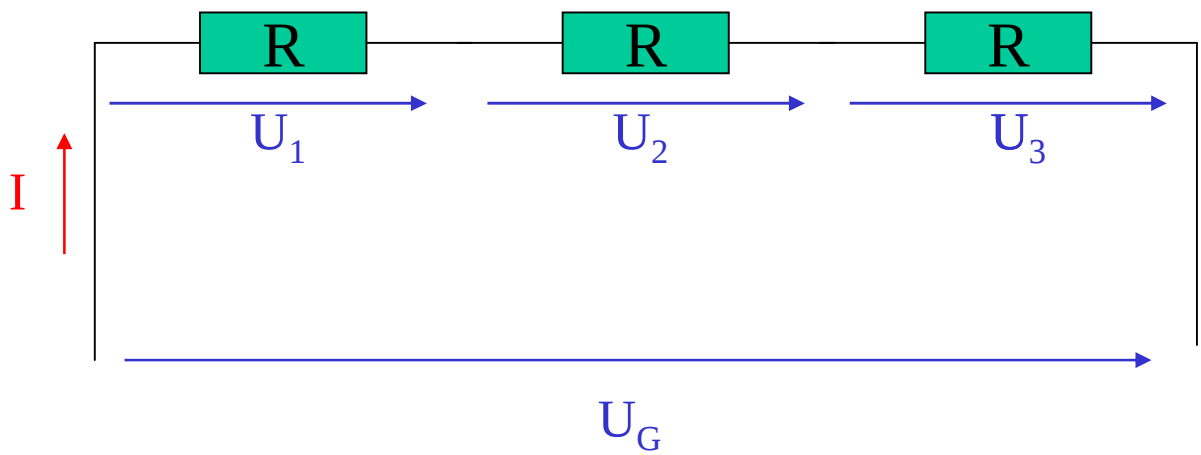

$$U_G = U_1 + U_2 + U_3$$

$$I = I = I$$